


Contents :

1. Introduction of Boost converter
2. Design Specifications of Boost Converter
 - Assumptions
 - Component Selection
3. Simulation and waveforms of Boost Converter
4. Conclusion

Introduction : Step-Up Converter (Boost Converter)

- It is a DC-DC converter which produces a higher average output voltage than the dc input voltage V_{dc} .
- It also steps down the output current and is also called current buck circuit
- Its main application is in regulated dc power supplies and regenerative braking of dc motors.
- It basically consists of a switch which is closed for a certain period of time t_{on} and open for a time t_{off} along with a high capacitor filter.
- The average output voltage value V_o depends on t_{on} and t_{off} .
- Pulse width modulation switching is used in which the switching duty ratio d is equal to ratio of on duration time to the time period of switch.

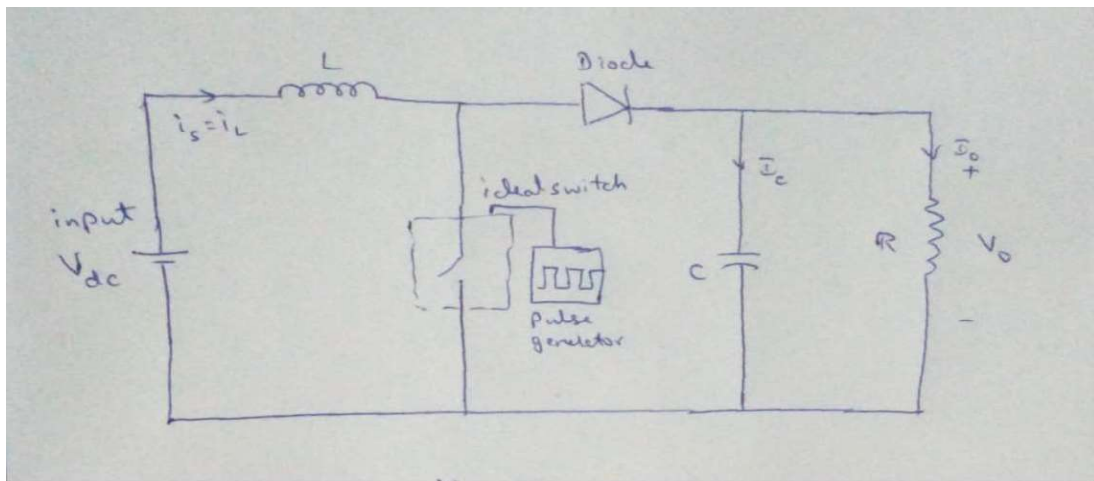Below is the basic circuit of a boost converter :



- As we know the average voltage across inductor is always zero, hence based on voltage time balance equation we get $V_o = V_{in}/(1-d)$
- As we know the average current through a capacitor is always zero, hence based on current time balance equation we get $I_o = I_{in}*(1-d)$
- The ripple in output current $\Delta I_L = V_o*(1-d)*d*T / L$
- The ripple in output voltage $\Delta V_o = V_o*d*T/R*C$

Design Specifications:

Assumptions :

- Assuming input voltage $V_{dc} = 20V$
- Switching frequency = 5K Hz
- Load Resistance $R_L = 10$ ohms
- Desired permissible Ripple in output current = 0.25 A
- Desired permissible Ripple in output voltage = 0.25 V
- Desired Output voltage = 50 V

Component Selection :

1. Switch : For simulation of boost converter we use ideal switch with zero internal resistance and which can operate in high switching frequency
2. Pulse Generator : We need pulse generator to produce gate pulses which can trigger the switch. The Time period of the pulse signals are assumed to be 5K Hz with 60% duty cycle calculated using

$$1/(1-d) = V_0(\text{Desired})/V_{dc}(\text{input})$$

$$1-d = 20/50$$

$$d = 0.6 = 60\%$$

3. Inductor : Inductor is chosen based on the permissible ripple allowed in output current.

$$L = V_o * (1-d) * d * T / \Delta I_L$$

Design

For inductor :- $f_s = 5 \text{ KHz} \Rightarrow T = 0.2 \text{ ms}$

$$\Delta I_L = \frac{V_o(1-d)dT}{L}$$
$$L = \frac{V_o(1-d)dT}{\Delta I_L}$$
$$L = \frac{5(1-0.6)0.6 \times 0.2 \times 10^{-3}}{0.25} = 9.6 \text{ mH}$$

$L = 9.6 \text{ mH}$

4. Capacitor : Capacitor is chosen based on the permissible ripple allowed in output voltage.

$$C = \frac{V_o \cdot d \cdot T}{R \cdot \Delta V_o}$$

For Capacitor:-

$$\Delta V_o = \frac{V_o \cdot D \cdot T}{R \cdot C}$$
$$C = \frac{V_o \cdot d \cdot T}{R \cdot \Delta V_o} = \frac{50 \times 0.6 \times 0.2 \times 10^{-3}}{10 \times 0.25}$$
$$C = 2.4 \text{ mF}$$

Simulation and waveforms:

Fig 1 : Circuit diagram of a boost converter

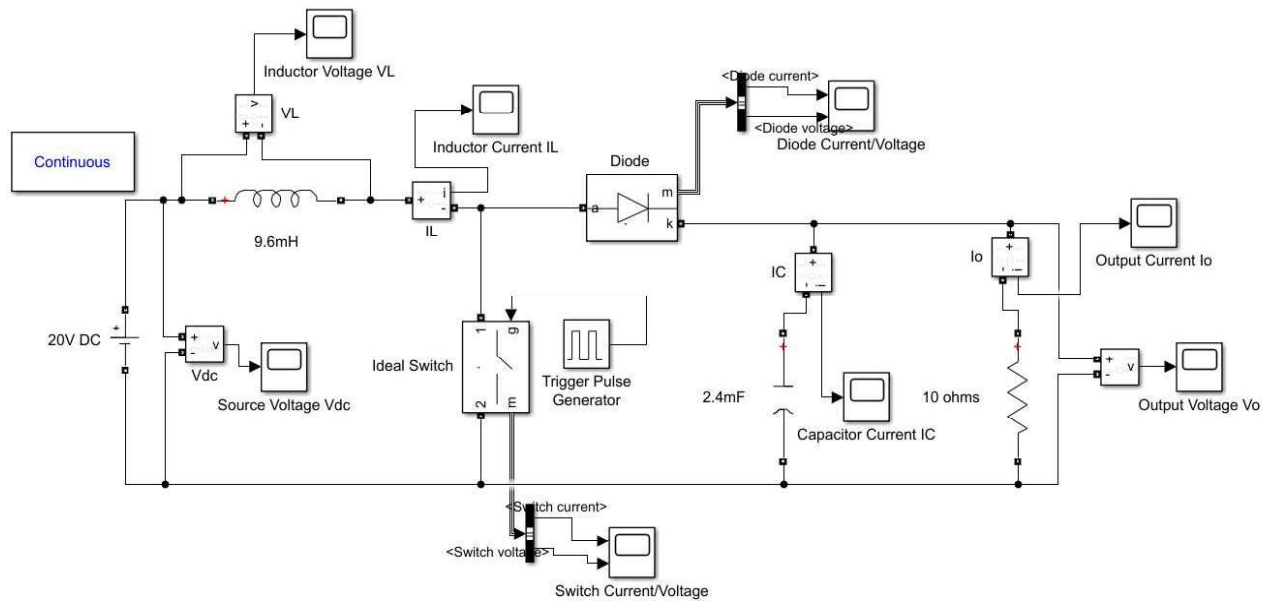


Fig 2 : Input DC Voltage source (Vdc)

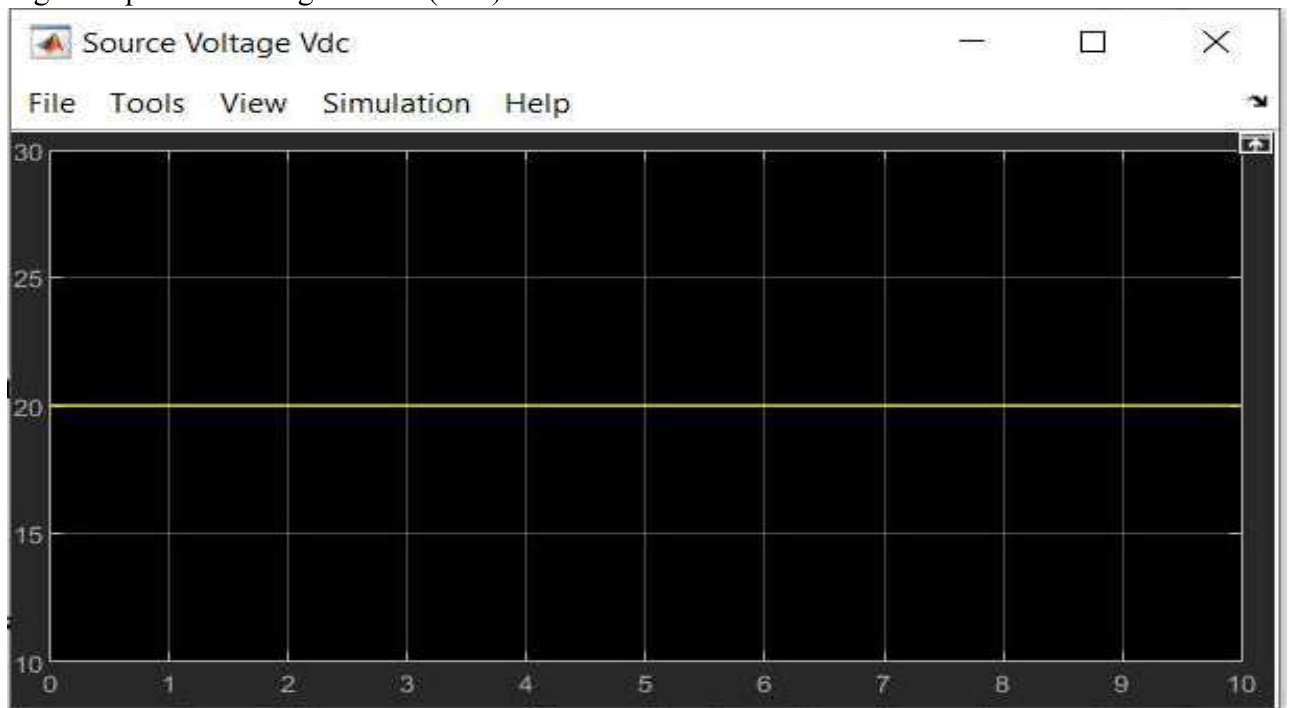


Fig 3 : Source Current waveform / Inductor Current I_L

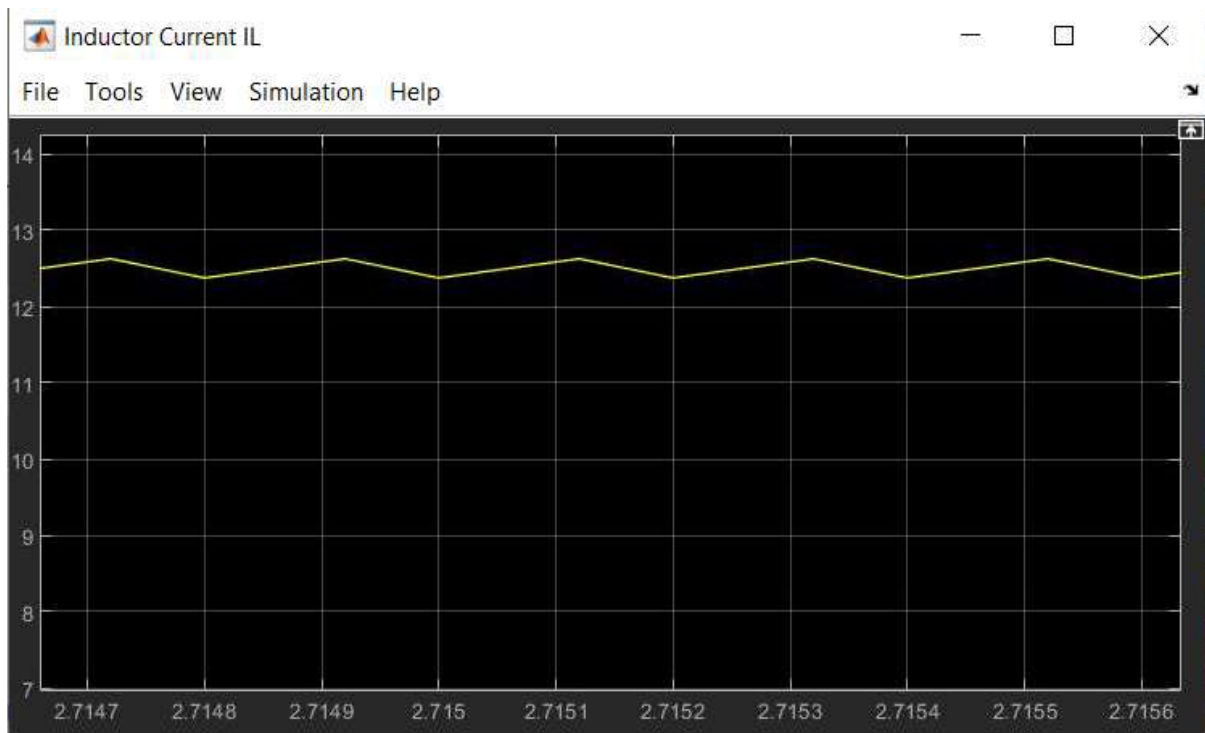


Fig 4 : Output Voltage waveform (V_o)

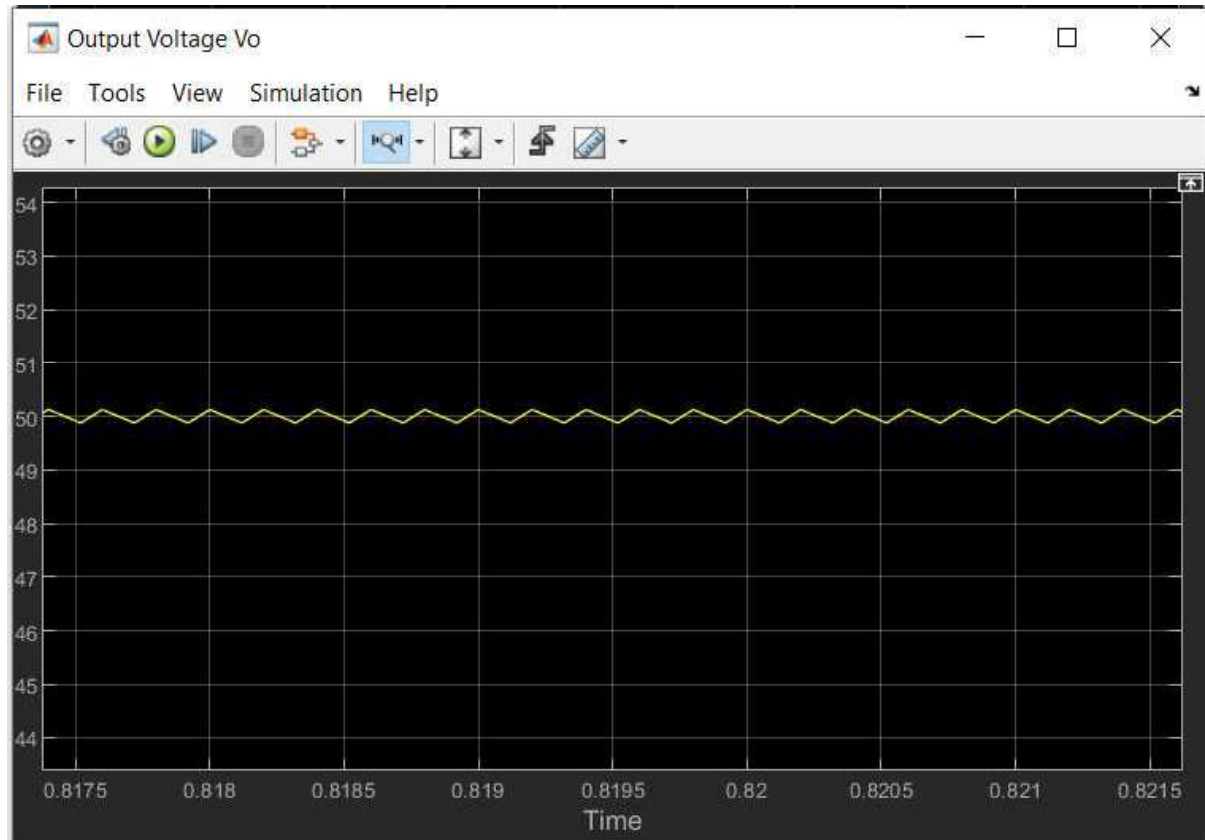


Fig 5 : Output current waveform (I_o)

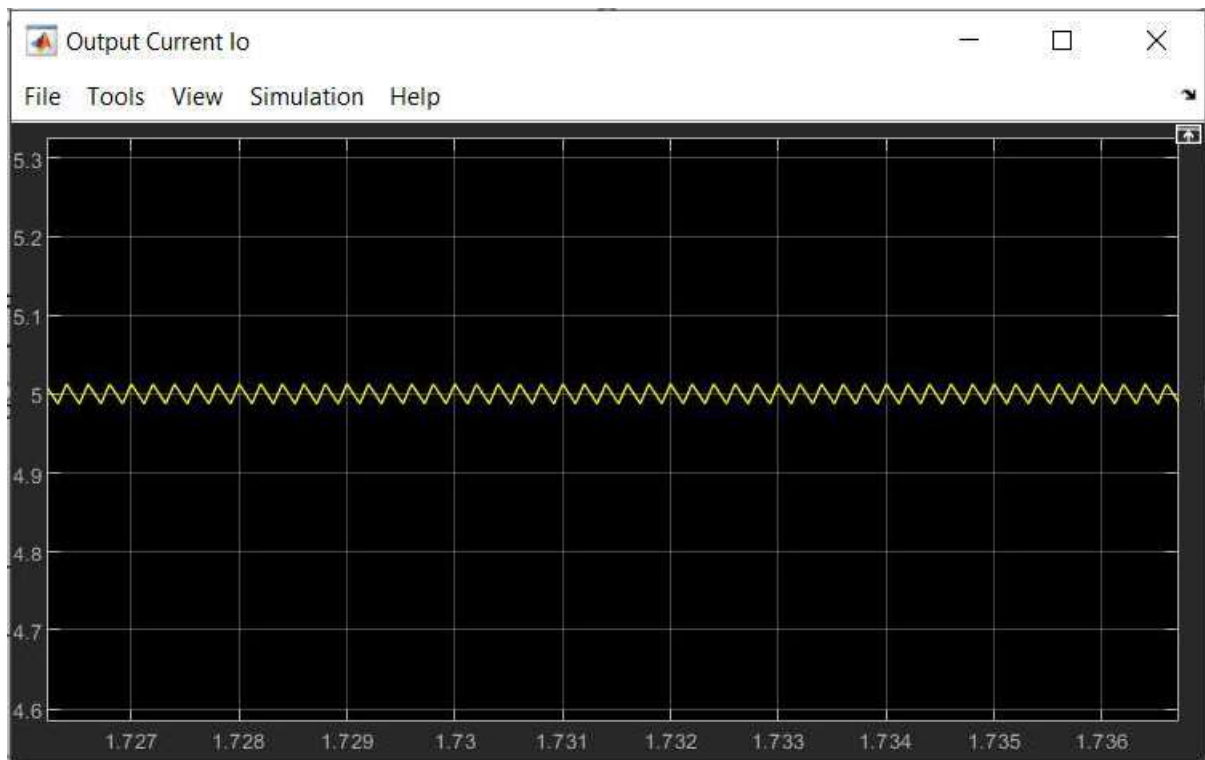


Fig 6 : Voltage across Inductor (V_L)

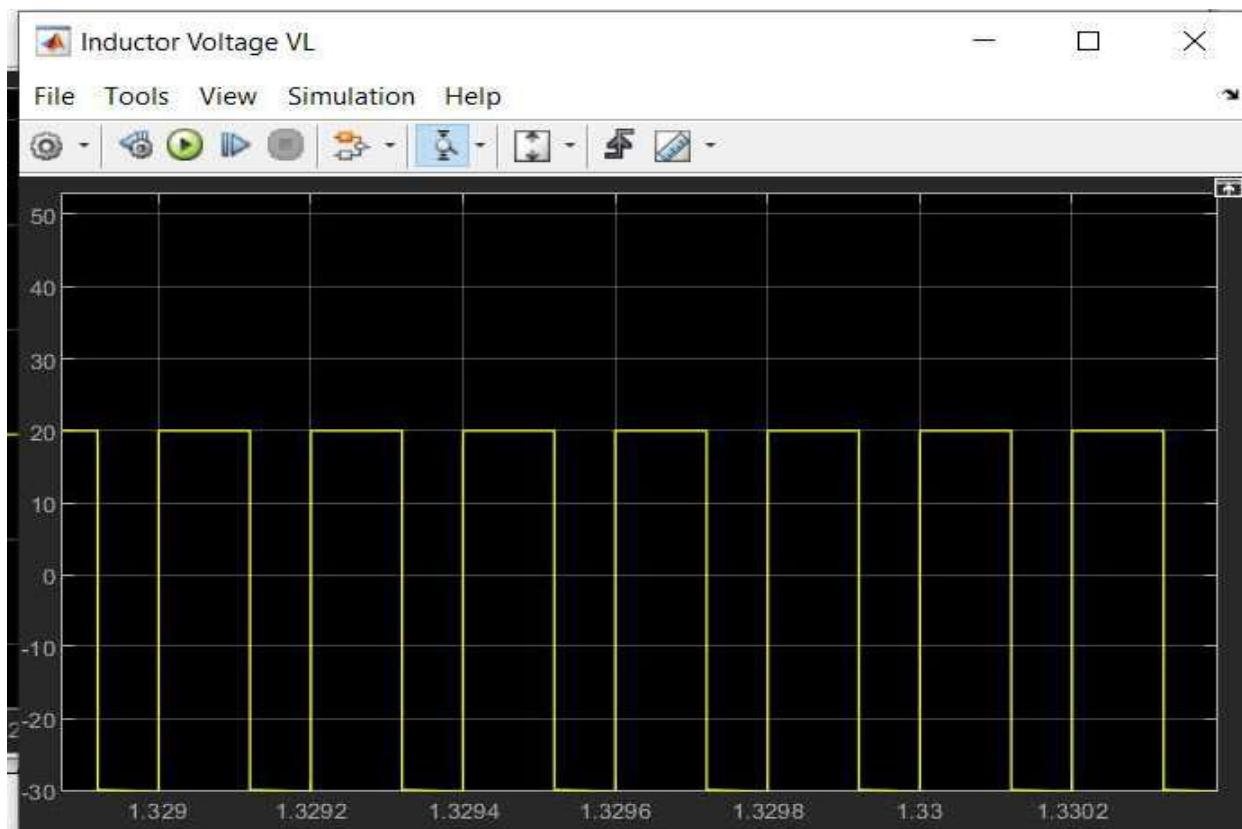


Fig 7 : Current through diode (I_{diode}) and Voltage across diode (V_{diode})

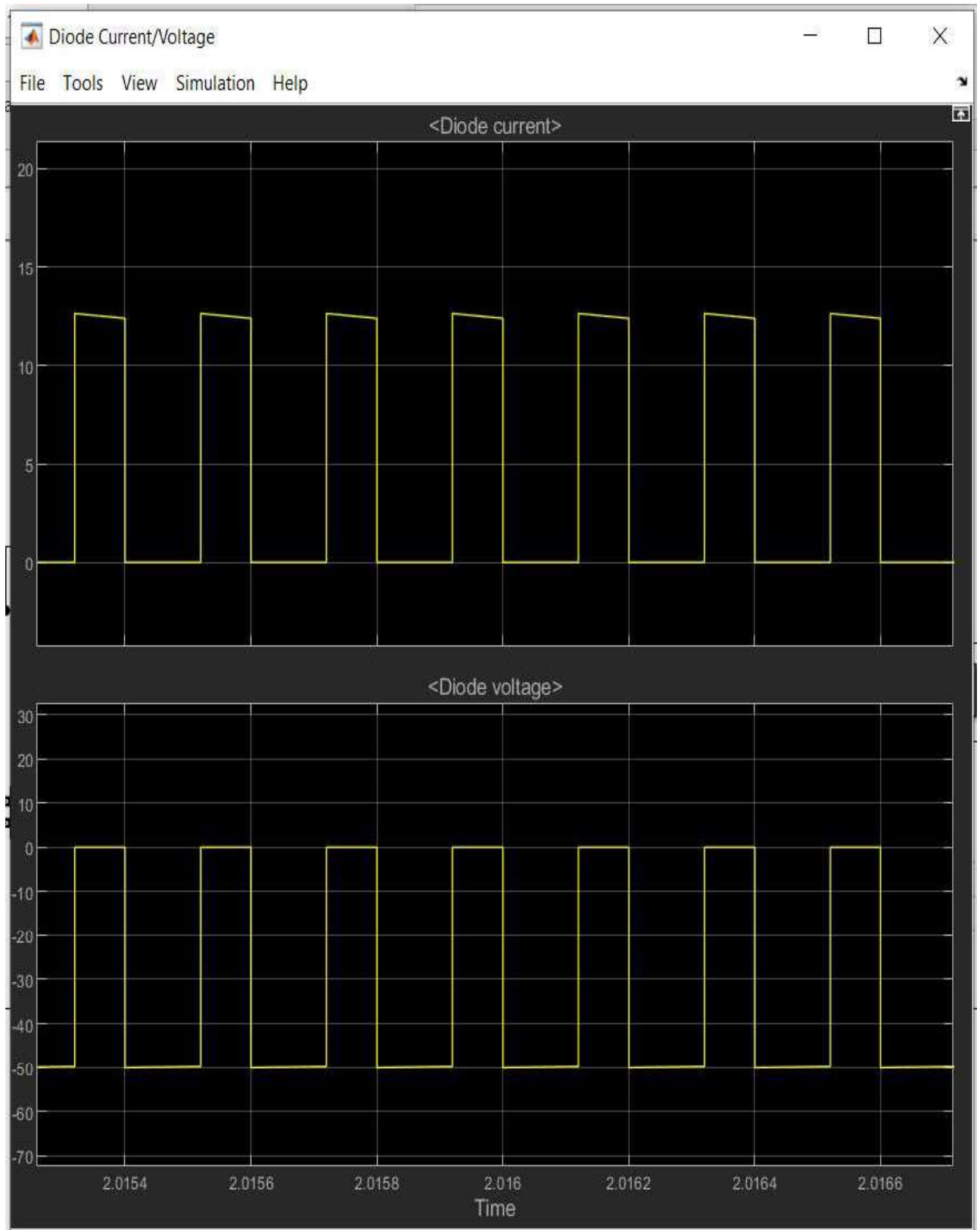


Fig 8 : Current through Switch and Voltage across switch


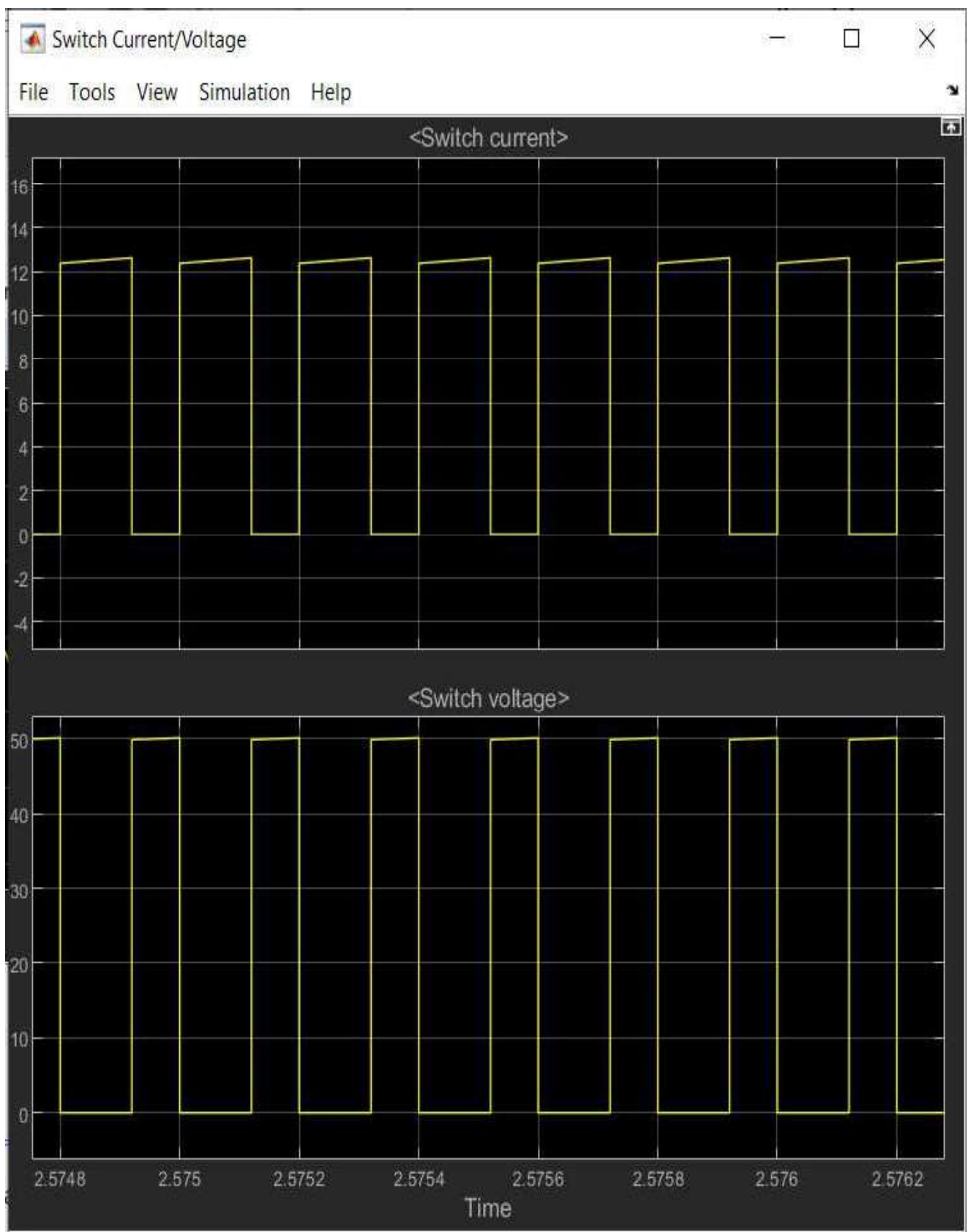


Fig 9 : Current through capacitor (I_c)

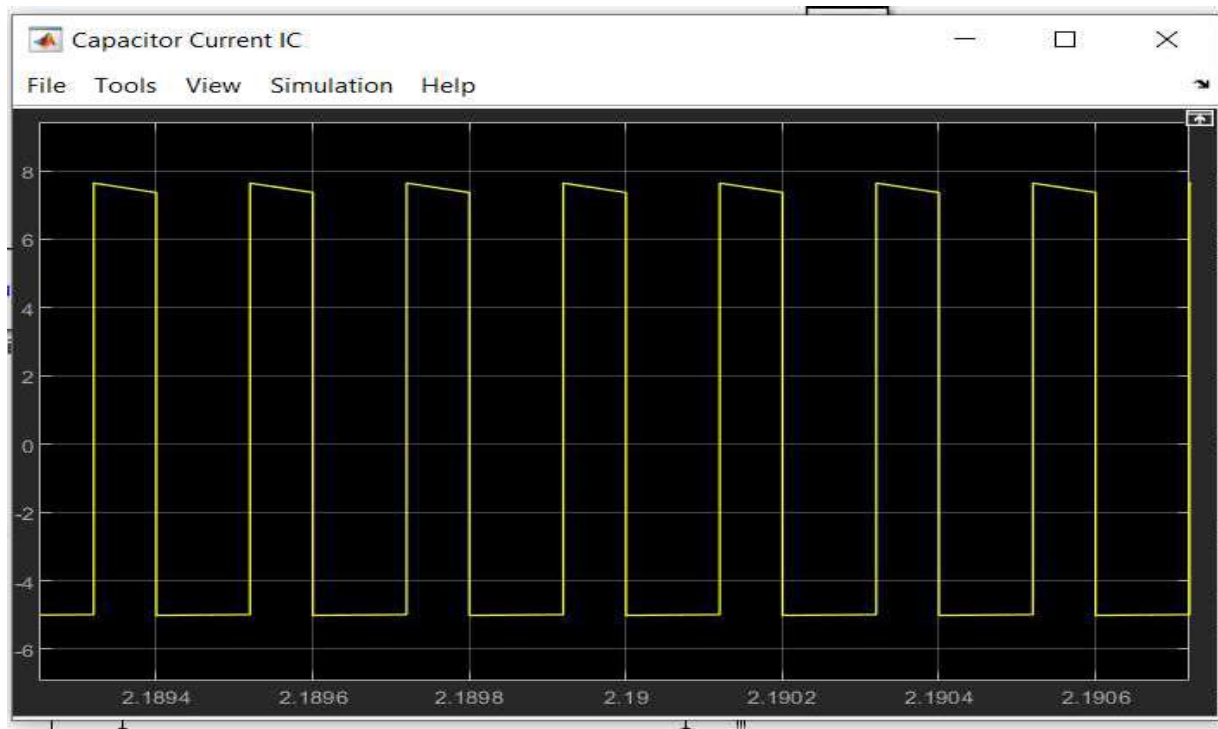

Conclusion :

Boost converter is simulated in Matlab and desired output is obtained.